

Lab 7 Register File


1 Bit Register

Verilog:

```
module Register1Bit(  
    input Din,  
    input Write,  
    input Clk,  
    input Clr,  
    output Dout  
);  
  
    wire d,q;  
  
    fd_c flipflop(q,Clk,d,Clr);  
    MUX21 mux(d,Write,q,Din);  
    assign Dout=q;  
  
endmodule
```

TCL:
 
```
wave add / -radix hex  
isim force add Clr 1  
isim force add Clk 0 -time 0 -value 1 -time 10ns -repeat 20ns  
isim force add Din 1  
isim force add Write 0  
run 33ns  
isim force add Clr 0  
run 40ns  
isim force add Write 1  
run 160ns
```




4 Bit Register:

Verilog:

```
module Register4Bit(  
    input [3:0] Din,  
    input Write,  
    input Clk,  
    input Clr,  
    output [3:0] Dout  
);  
    Register1Bit r0(Din[0], Write, Clk, Clr, Dout[0]);  
    Register1Bit r1(Din[1], Write, Clk, Clr, Dout[1]);  
    Register1Bit r2(Din[2], Write, Clk, Clr, Dout[2]);  
    Register1Bit r3(Din[3], Write, Clk, Clr, Dout[3]);  
endmodule
```

TCL:
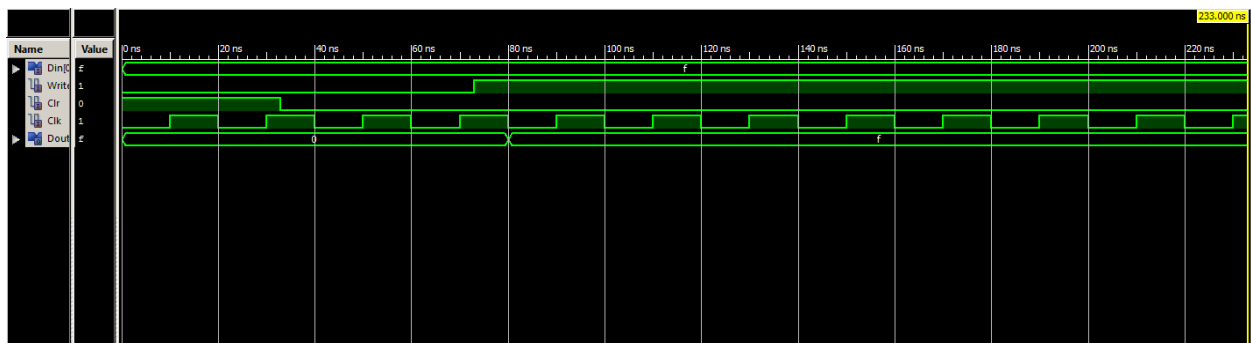
```
wave add / -radix hex  
isim force add Clr 1  
isim force add Clk 0 -time 0 -value 1 -time 10ns -repeat 20ns  
isim force add Din 1111  
isim force add Write 0  
run 33ns  
isim force add Clr 0  
run 40ns  
isim force add Write 1  
run 160ns
```



2 to 4 Decoder:

Verilog:

```
module Decoder2_4(  
    input Addr0,  
    input Addr1,  
    output Sel0,  
    output Sel1,  
    output Sel2,  
    output Sel3  
);  
    wire nAddr0, nAddr1;  
    not(nAddr0,Addr0);  
    not(nAddr1, Addr1);  
    and(Sel3,Addr0,Addr1);  
    and(Sel2,nAddr0,Addr1);  
    and(Sel1,Addr0,nAddr1);  
    and(Sel0,nAddr0,nAddr1);  
endmodule
```


TCL:

wave add / -radix hex

isim force add Addr0 0 -time 0 -value 1 -time 10ns -repeat 20ns

isim force add Addr1 0 -time 0 -value 1 -time 20ns -repeat 40ns

run 160ns

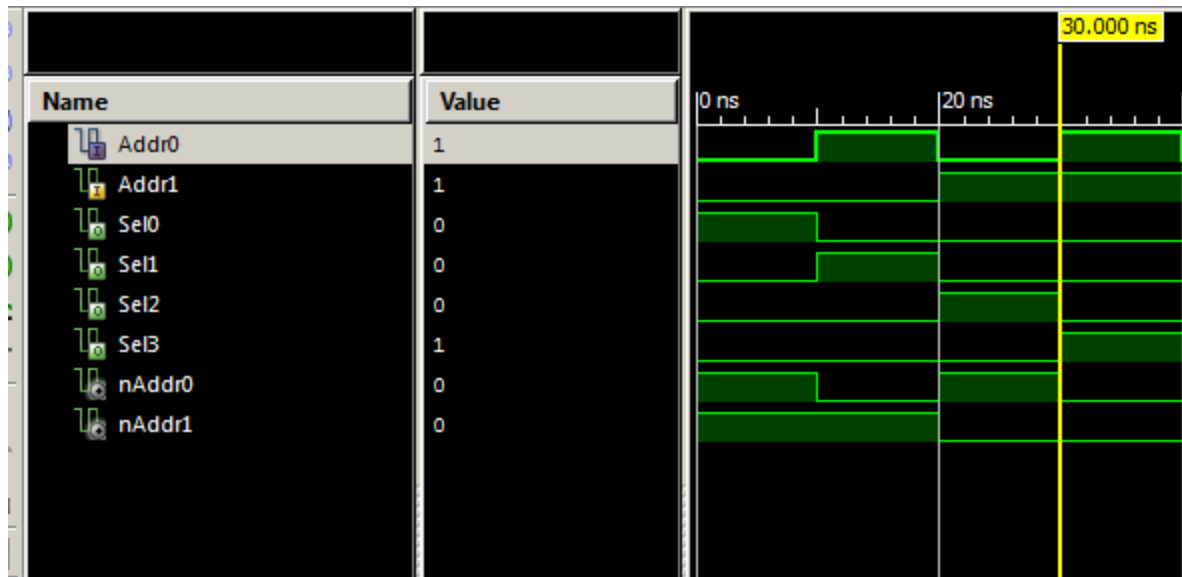


4 Bit 4 Word:

Verilog:

```
module Register4Word(  
  
    input [0:3] Din,  
    input Write,  
    input Clk,  
    input Clr,  
    input Addr0,  
    input Addr1,  
    output [3:0] Reg_0,  
    output [3:0] Reg_1,  
    output [3:0] Reg_2,  
    output [3:0] Reg_3  
);  
    wire wReg0, wReg1, wReg2, wReg3, Sel0, Sel1, Sel2, Sel3;  
    Decoder2_4 decoder(Addr0, Addr1, Sel0, Sel1, Sel2, Sel3);  
    and(wReg3, Write, Sel3);  
    and(wReg2, Write, Sel2);  
    and(wReg1, Write, Sel1);  
    and(wReg0, Write, Sel0);  
    Register4Bit reg3(Din,wReg3,Clk,Clr,Reg_3);  
    Register4Bit reg2(Din,wReg2,Clk,Clr,Reg_2);  
    Register4Bit reg1(Din,wReg1,Clk,Clr,Reg_1);  
    Register4Bit reg0(Din,wReg0,Clk,Clr,Reg_0);  
endmodule
```

TCL:
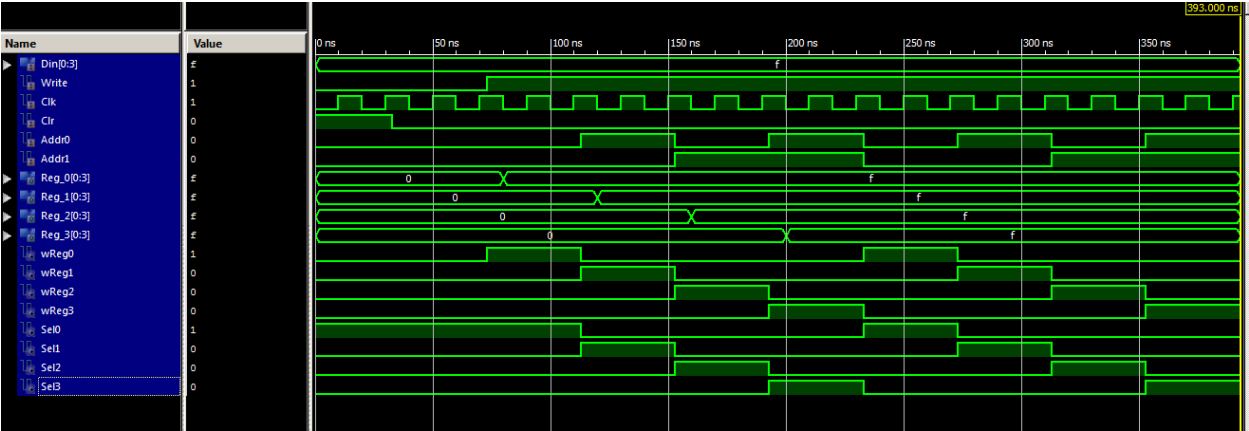
```
wave add / -radix hex  
isim force add Clr 1  
isim force add Din 1111  
isim force add Write 0  
isim force add Addr0 0  
isim force add Addr1 0  
run 33ns  
isim force add Clr 0  
run 40ns  
isim force add Write 1  
isim force add Addr0 0 -time 0 -value 1 -time 40ns -repeat 80ns  
isim force add Addr1 0 -time 0 -value 1 -time 80ns -repeat 160ns  
run 320ns
```



4 to 1 and 16 to 4 Bit MUX:

Verilog:

```
module mux4_1(result, sel, Din);
```

```
    input[1:0] sel;
```

```
    input[3:0] Din;
```

```
    output result;
```

```
    wire r0,r1;
```

```
    mux2_1 m0(r0, sel[0], Din[0], Din[1]);
```

```
                                mux2_1 m1(r1, sel[0], Din[2], Din[3]);
```

```
                                mux2_1 m2(result, sel[1], r0, r1);
```

```
endmodule
```

```
module mux16_4(result, sel, Din3, Din2, Din1, Din0);
```

```
    input[0:1] sel;                // 2 select line
```

```
    input[3:0] Din3, Din2, Din1, Din0;    // 4 4-bit values come in as inputs
```

```
    output[3:0] result;              // 4-bit output
```

```
    // Select which bits of which input gets passed to which of the 4-bit muxes
```

```
    mux4_1 M3(result[3], sel, {Din3[3], Din2[3], Din1[3], Din0[3]});
```

```
    mux4_1 M2(result[2], sel, {Din3[2], Din2[2], Din1[2], Din0[2]});
```

```
    mux4_1 M1(result[1], sel, {Din3[1], Din2[1], Din1[1], Din0[1]});
```

```
    mux4_1 M0(result[0], sel, {Din3[0], Din2[0], Din1[0], Din0[0]});
```

```
endmodule
```

TCL:

```
wave add / -radix hex
```

```
isim force add Din3 1010
```


```
isim force add Din2 1100
```

```
isim force add Din1 0101
```

```
isim force add Din0 0011
```

```
isim force add sel 00 -time 0 -value 01 -time 20ns -value 10 -time 40ns -value 11 -time 60ns -repeat 80ns
```

```
run 160ns
```

 

Complete Register:

Verilog:

```
module Register4Word4Bit(
    input [3:0] Din,
    input Write,
    input Clk,
    input Clr,
    input Addr0,
    input Addr1,
    input [1:0] ReadAddr,
    output [3:0] RegFile_out,
    output [3:0] Din_led
);

wire [3:0] Reg_0, Reg_1, Reg_2, Reg_3;
Register4Word fourWordReg(Din, Write, Clk, Clr, Addr0, Addr1, Reg_0, Reg_1, Reg_2, Reg_3);
mux16_4 mux(RegFile_out, ReadAddr, Reg_3, Reg_2, Reg_1, Reg_0);
buf(Din_led[3],Din[3]);
buf(Din_led[2],Din[2]);
buf(Din_led[1],Din[1]);
buf(Din_led[0],Din[0]);

endmodule
```

UCF:

```
## clock pin for Nexys 2 Board
NET Clk LOC = "B8"; # Bank = 0, Pin name = IP_L13P_0/GCLK8, Type = GCLK, Sch name = GCLK0
## Leds
NET RegFile_out<0> LOC = "J14"; # Bank = 1, Pin name = IO_L14N_1/A3/RHCLK7, Type = RHCLK/DUAL,
Sch name = JD10/LD0
NET RegFile_out<1> LOC = "J15"; # Bank = 1, Pin name = IO_L14P_1/A4/RHCLK6, Type = RHCLK/DUAL,
Sch name = JD9/LD1
NET RegFile_out<2> LOC = "K15"; # Bank = 1, Pin name = IO_L12P_1/A8/RHCLK2, Type = RHCLK/DUAL,
Sch name = JD8/LD2
NET RegFile_out<3> LOC = "K14"; # Bank = 1, Pin name = IO_L12N_1/A7/RHCLK3/TRDY1, Type =
RHCLK/DUAL, Sch name = JD7/LD3
NET Din_led<0> LOC = "E17"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD4
NET Din_led<1> LOC = "P15"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD5
NET Din_led<2> LOC = "F4"; # Bank = 3, Pin name = IO, Type = I/O, Sch name = LD6
NET Din_led<3> LOC = "R4"; # Bank = 3, Pin name = IO/VREF_3, Type = VREF, Sch name = LD7
```

Switches

NET ReadAddr<0> LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0
NET ReadAddr<1> LOC = "H18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = SW1
NET Addr0 LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2
NET Addr1 LOC = "K17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3
NET Din<0> LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4
NET Din<1> LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5
NET Din<2> LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6
NET Din<3> LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7

Buttons

NET Clr LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN0
#NET "btn<1>" LOC = "D18"; # Bank = 1, Pin name = IP/VREF_1, Type = VREF, Sch name = BTN1
#NET "btn<2>" LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN2
NET Write LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN3