

Ty Madsen  
ECEN 220  
9 October 2013

### Lab #5 - Arithmetic Logic Unit

MUX 4:1:

VERILOG:

```
module MUX41(  
    input A,  
    input Sum,  
    input AandB,  
    input Anot,  
    input [1:0] control,  
    output Result  
);  
    wire out;  
    assign Result= control == 2'b00 ? A :  
    control == 2'b01 ? Sum :  
    control == 2'b10 ? AandB :  
    Anot;
```

Endmodule

TCL:

wave add / -radix hex


isim force add A 0 -time 0 -value 1 -time 10ns -repeat 20ns

isim force add Sum 0 -time 0 -value 1 -time 20ns -repeat 40ns

isim force add AandB 0 -time 0 -value 1 -time 40ns -repeat 80ns

isim force add Anot 0 -time 0 -value 1 -time 80ns -repeat 160ns

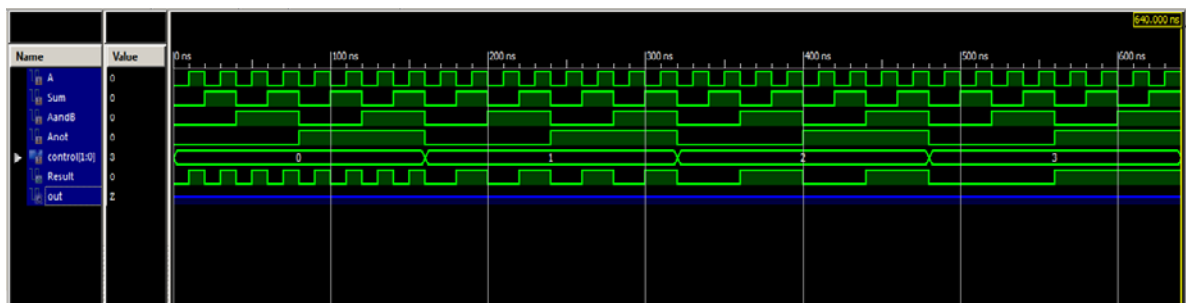isim force add control 00 -time 0 -value 01 -time 160ns -value 10 -time 320ns -value 11 -time 480ns



Full Adder:

VERILOG:

```
module FullAdder(
    input A,
    input B,
    input Cin,
    output Sum,
    output Cout
);
    wire An,Bn,Cn,ABnCn,AnBnC,ABC,AnBCn,CB,AB,AC;

    not(An,A);
    not(Bn,B);
    not(Cn,Cin);
    and(ABnCn,A,Bn,Cn);
    and(AnBnC,An,Bn,Cin);
    and(ABC,A,B,Cin);
    and(AnBCn,An,B,Cn);
    or(Sum,ABnCn,AnBnC,ABC,AnBCn);

    and(AB,A,B);
    and(AC,A,Cin);
    and(CB,Cin,B);
    or(Cout,AB,AC,CB);

endmodule
```


TCL:

wave add / -radix hex

isim force add A 0 -time 0 -value 1 -time 10ns -repeat 20ns

isim force add B 0 -time 0 -value 1 -time 20ns -repeat 40ns

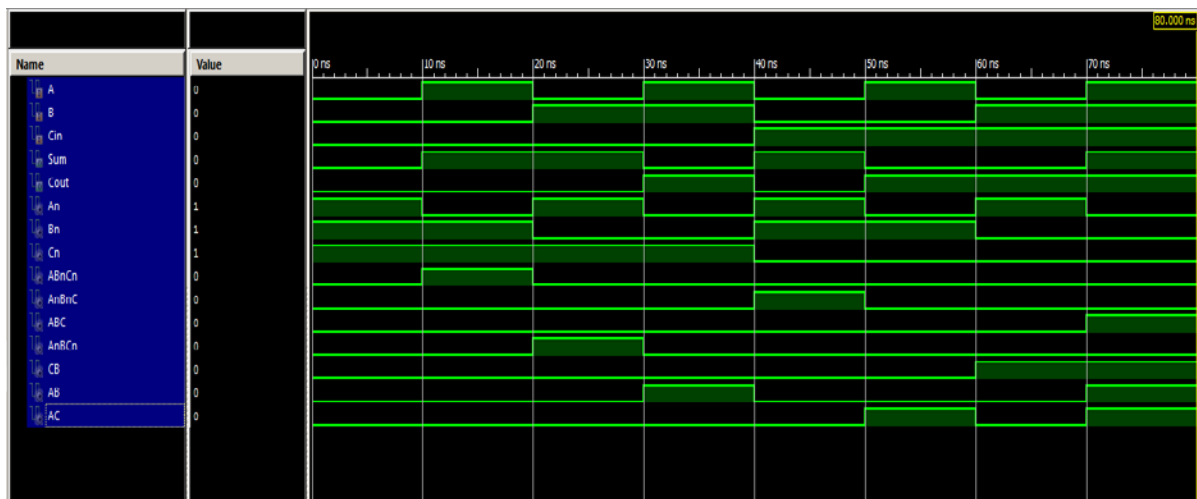isim force add Cin 0 -time 0 -value 1 -time 40ns -repeat 80ns



1 Bit ALU:

VERILOG:

```
module OneBitALU(  
    input A,  
    input B,  
    input Cin,  
    input [1:0] control,  
    output Result,  
    output Cout  
);  
    wire FASum, FACout,AandB,Anot;  
    and(AandB,A,B);  
    not(Anot,A);  
    FullAdder FullAdd(A,B,Cin,FASum,FACout);  
    assign Cout = control == 2'b01 ? FACout : 0;  
    MUX41 Multiplexor(A,FASum,AandB,Anot,control,Result);  
Endmodule
```

Endmodule

TCL:


wave add / -radix hex

isim force add A 0 -time 0 -value 1 -time 10ns -repeat 20ns

isim force add B 0 -time 0 -value 1 -time 20ns -repeat 40ns

isim force add Cin 0 -time 0 -value 1 -time 40ns -repeat 80ns

 isim force add control 00 -time 0 -value 01 -time 80ns -value 10 -time 160ns -value 11 -time 240ns -  
repeat 320ns



4 Bit ALU:

VERILOG:

```
module FourBitALU(  
    input [3:0] A,  
    input [3:0] B,  
    input Cin,  
    input [1:0] control,  
    output [3:0] Result,  
    output Cout  
);  
    wire Cout1,Cout2,Cout3,R1,R2,R3,R4;  
    OneBitALU A0(A[0],B[0],1'b0,control,R1,Cout1);  
    OneBitALU A1(A[1],B[1],Cout1,control,R2,Cout2);  
    OneBitALU A2(A[2],B[2],Cout2,control,R3,Cout3);  
    OneBitALU A3(A[3],B[3],Cout3,control,R4,Cout);  
    assign Result[0] = R1;  
    assign Result[1] = R2;  
    assign Result[2] = R3;  
    assign Result[3] = R4;  
  
endmodule
```

TCL:


wave add / -radix hex

isim force add Cin 0

isim force add control 00 -time 0 -value 01 -time 10ns -value 10 -time 20ns -value 11 -time 30ns -repeat 40ns

isim force add A 0000 -time 0 -value 1111 -time 40ns -repeat 80ns

 isim force add B 0000 -time 0 -value 1111 -time 80ns -repeat 160ns



UCF:

#### ## Leds

NET Result<0> LOC = "J14"; # Bank = 1, Pin name = IO\_L14N\_1/A3/RHCLK7, Type = RHCLK/DUAL, Sch name = JD10/LD0

NET Result<1> LOC = "J15"; # Bank = 1, Pin name = IO\_L14P\_1/A4/RHCLK6, Type = RHCLK/DUAL, Sch name = JD9/LD1

NET Result<2> LOC = "K15"; # Bank = 1, Pin name = IO\_L12P\_1/A8/RHCLK2, Type = RHCLK/DUAL, Sch name = JD8/LD2

NET Result<3> LOC = "K14"; # Bank = 1, Pin name = IO\_L12N\_1/A7/RHCLK3/TRDY1, Type = RHCLK/DUAL, Sch name = JD7/LD3

#NET "Led<4>" LOC = "E17"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD4

#NET "Led<5>" LOC = "P15"; # Bank = 1, Pin name = IO, Type = I/O, Sch name = LD5

#NET "Led<6>" LOC = "F4"; # Bank = 3, Pin name = IO, Type = I/O, Sch name = LD6

NET Cout LOC = "R4"; # Bank = 3, Pin name = IO/VREF\_3, Type = VREF, Sch name = LD7

#### ## Switches

NET B<0> LOC = "G18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW0

NET B<1> LOC = "H18"; # Bank = 1, Pin name = IP/VREF\_1, Type = VREF, Sch name = SW1

NET B<2> LOC = "K18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW2

NET B<3> LOC = "K17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW3

NET A<0> LOC = "L14"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW4

NET A<1> LOC = "L13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW5

NET A<2> LOC = "N17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW6

NET A<3> LOC = "R17"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = SW7

#### ## Buttons

#NET "btn<0>" LOC = "B18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN0

#NET "btn<1>" LOC = "D18"; # Bank = 1, Pin name = IP/VREF\_1, Type = VREF, Sch name = BTN1

NET control<0> LOC = "E18"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN2

NET control<1> LOC = "H13"; # Bank = 1, Pin name = IP, Type = INPUT, Sch name = BTN3

ANOMALIES:

None found